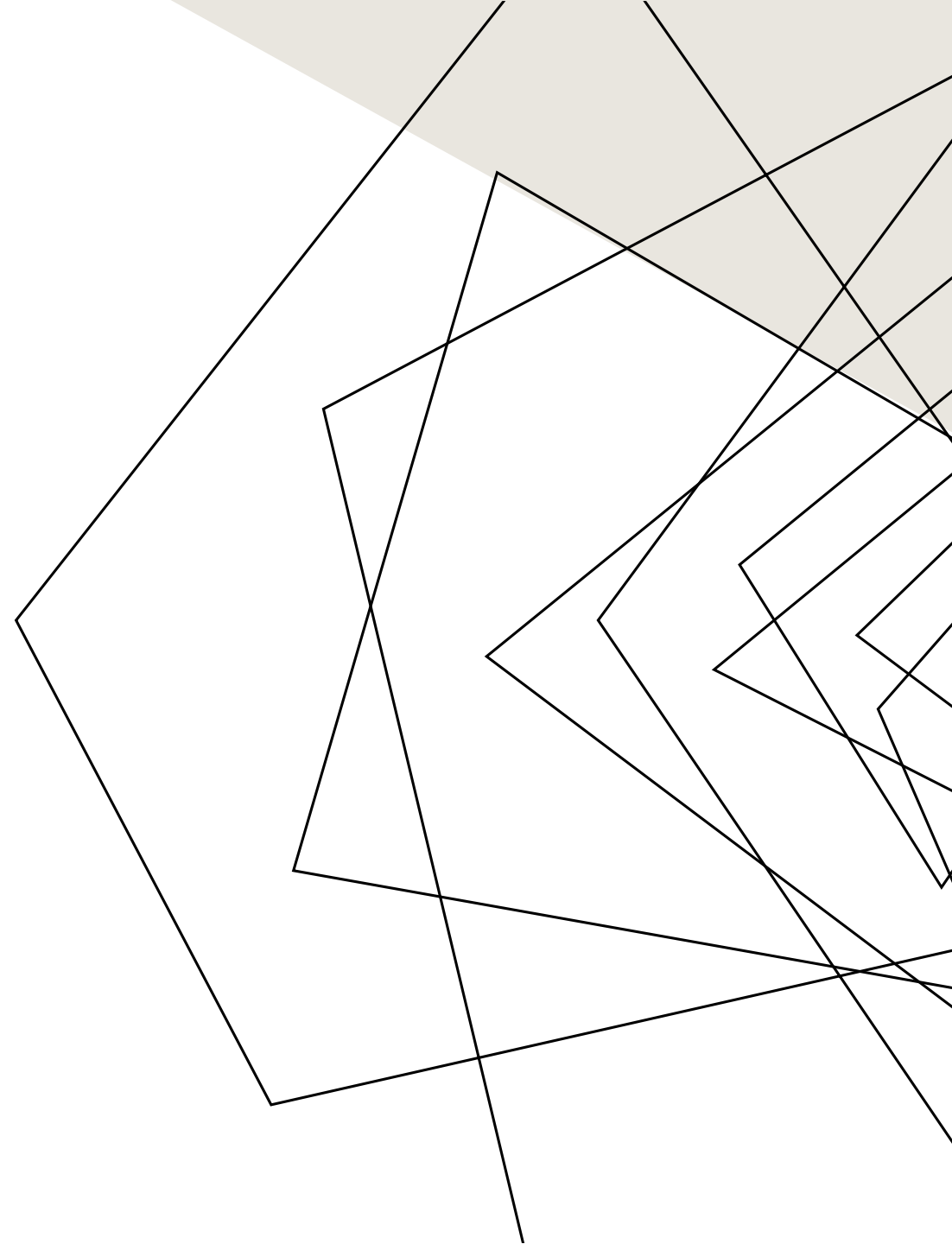



EW – II PROJECT REPORT

By

Aikya Oruganti (2023102062)

Indira C Reddy (2023102070)



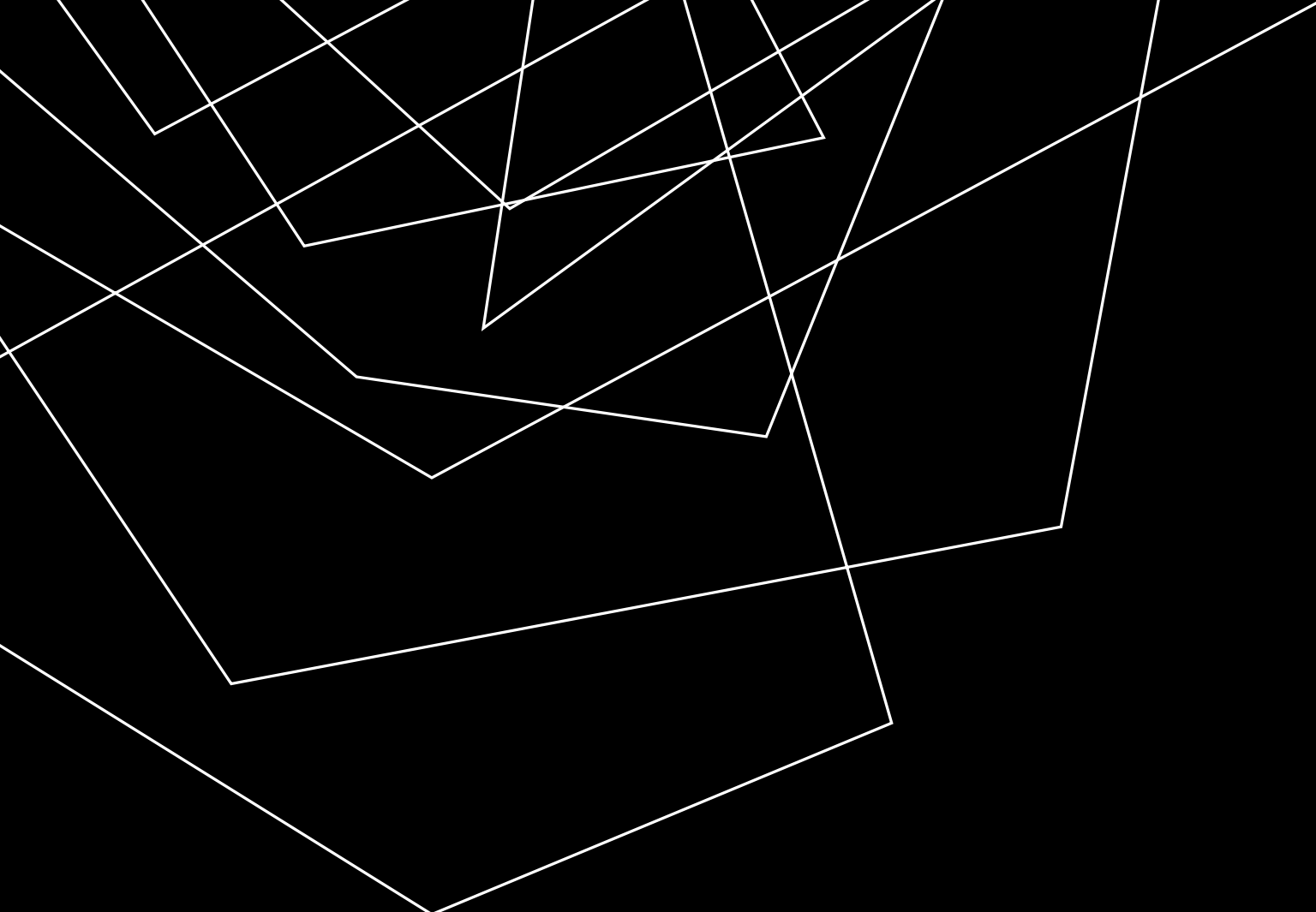


AUDIO AMPLIFIER



PROJECT OVERVIEW

- The aim of this project is to design and develop an audio amplifier that strengthens low power sound signals and drives an 10Ω speaker within a power budget of 0.5W.
- The amplifier is constructed based on several stages, each having a significant contribution towards signal amplification, filtering, and the delivery of power.
- The four stages include -
 - Pre-Amplifier Stage – Amplifies low signals while decreasing noise.
 - Gain Stage – Adds further voltage amplification.
 - Filter Stage – Permits only the specified frequency range to pass. In our case audio signals, ranging from 20Hz to 20kHz.
 - Power Amplifier Stage – Provides enough current and voltage to drive the speaker effectively.

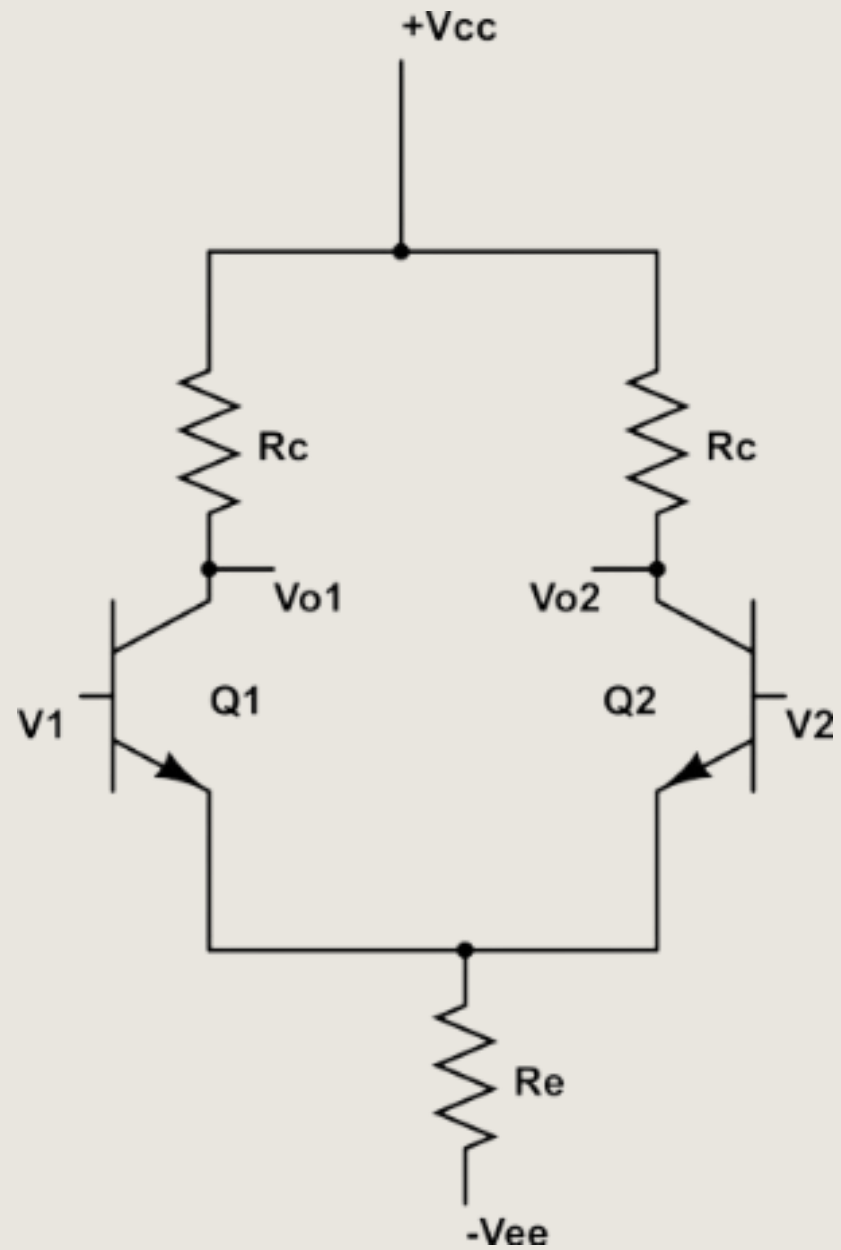

PRE – AMPLIFIER
STAGE

WORKING PRINCIPLE

- A differential amplifier in common mode
- The input received from mic is very weak(a few mV) so it is necessary to remove noise to maintain the signal. This also helps in matching impedances with next stage.
- Noise in grounded input and actual input are out of phase so they get cancelled.
- It amplifies the signal enough to let it be amplified by gain stage.
- Configuration used is Single Input Balanced Output (SISO)

CALCULATIONS

$$\text{gain} = -g_m R_c$$

$$\text{Gain} = \left(\frac{I_c}{V_T} \right) \left(\frac{R_c}{2} \right)$$

$$\frac{I_c}{I_s} = e^{V_{BE}/V_T}$$

$$\frac{I_c}{I_s} = 2.39 \times 10^{-14} \times e^{0.72/0.026}$$

$$\frac{I_c}{I_s} = 268.75 \times 10^{-16} \times 10^{10}$$

$$I_c = 268.75 \mu A$$

$$\text{gain} = -g_m R_c$$

$$11 = \frac{268.75 \times 10^{-6}}{26 \times 10^{-3}} \times \frac{R_c}{2}$$



$$11 \times 10^3 = 5.168 \times R_c$$

$$R_c = 2.92 \text{ k}\Omega \approx 3 \text{ k}\Omega \quad \boxed{R_c = 3 \text{ k}\Omega}$$


$$I_c = \frac{V_{CC} - V_{CE}}{2R_E} \quad \begin{matrix} 5V \\ \swarrow \\ 268.75 \mu A \end{matrix} \quad \begin{matrix} \searrow \\ 0.7V \end{matrix}$$


$$R_E \leq 12.08 \text{ k}\Omega$$
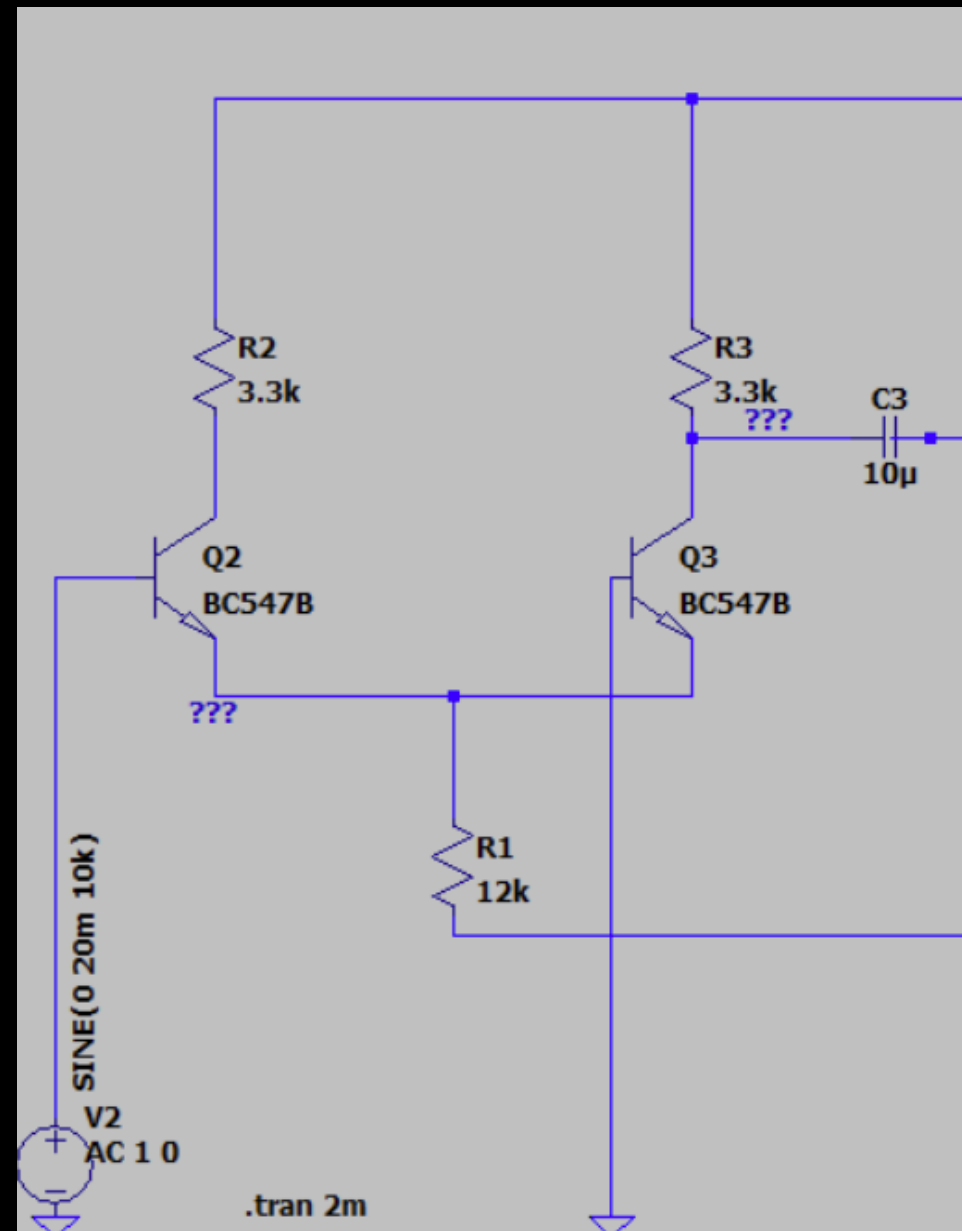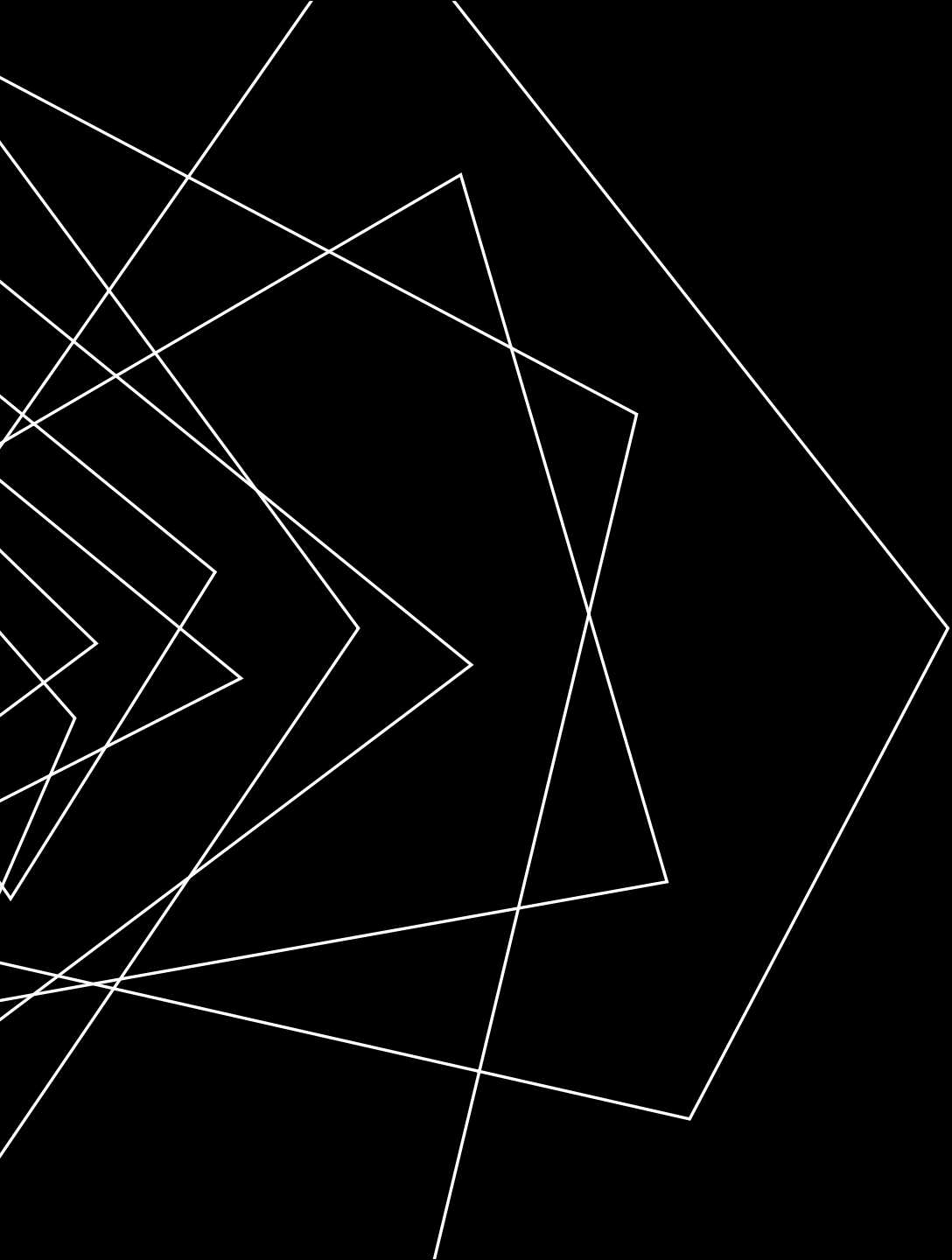
$$\therefore \boxed{R_E = 12 \text{ k}\Omega}$$



LTSPICE

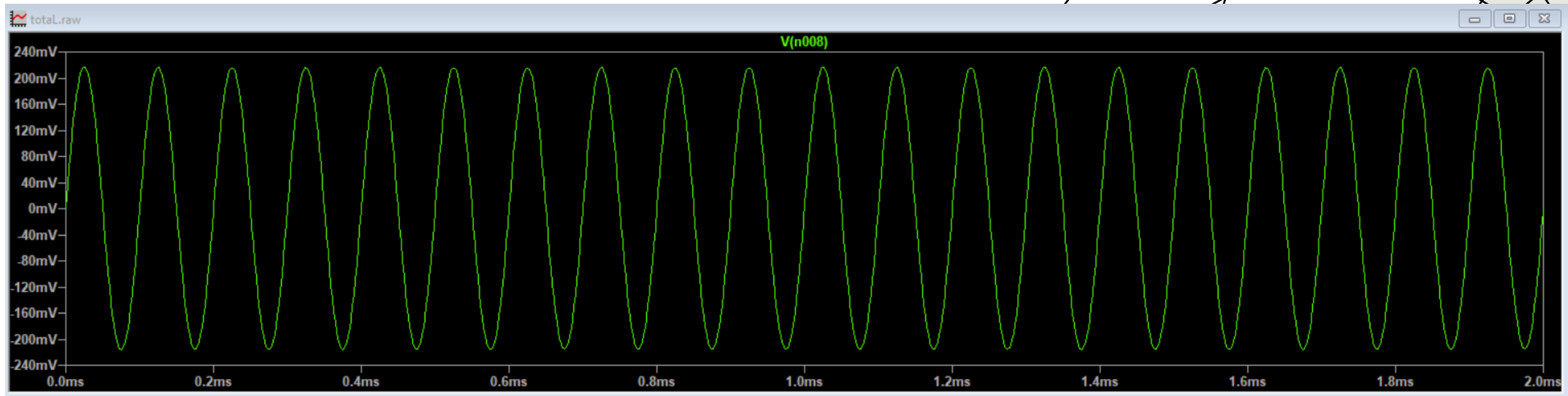

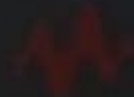

KEYSIGHT

EDUX1052G

Digital Storage Oscilloscope

50 MHz

1 10.0V/ 2 100V/


0.0s

20.00%/

Stop

f

1 -825V

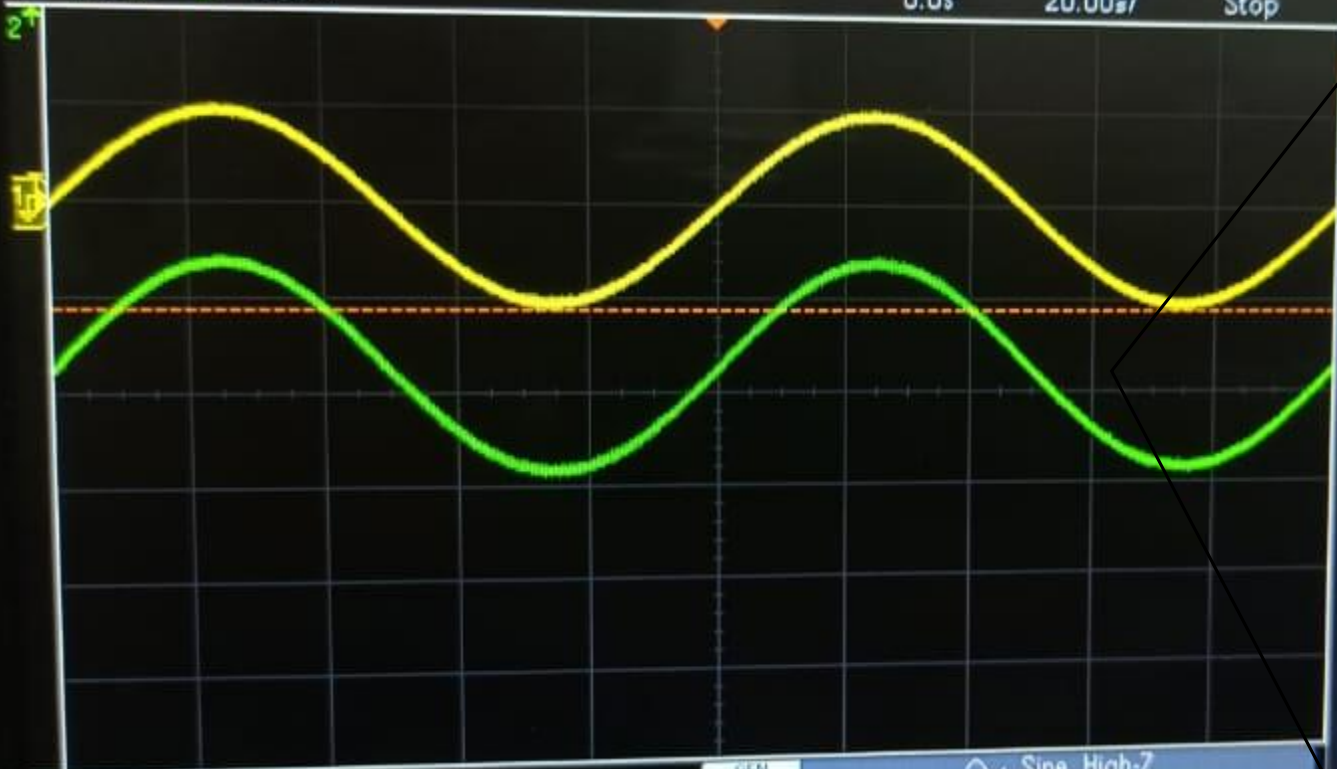

KEYSIGHT
TECHNOLOGIES

Wave Gen

Waveform

~ Sine

Frequency

10.00kHz

Amplitude

20.0mVpp

Offset

0.1V

Settings

Pk-Pk(1):

21.3mV

Pk-Pk(2):


233mV

Min(2):

-1.851V

Min(1):

-11.6mV

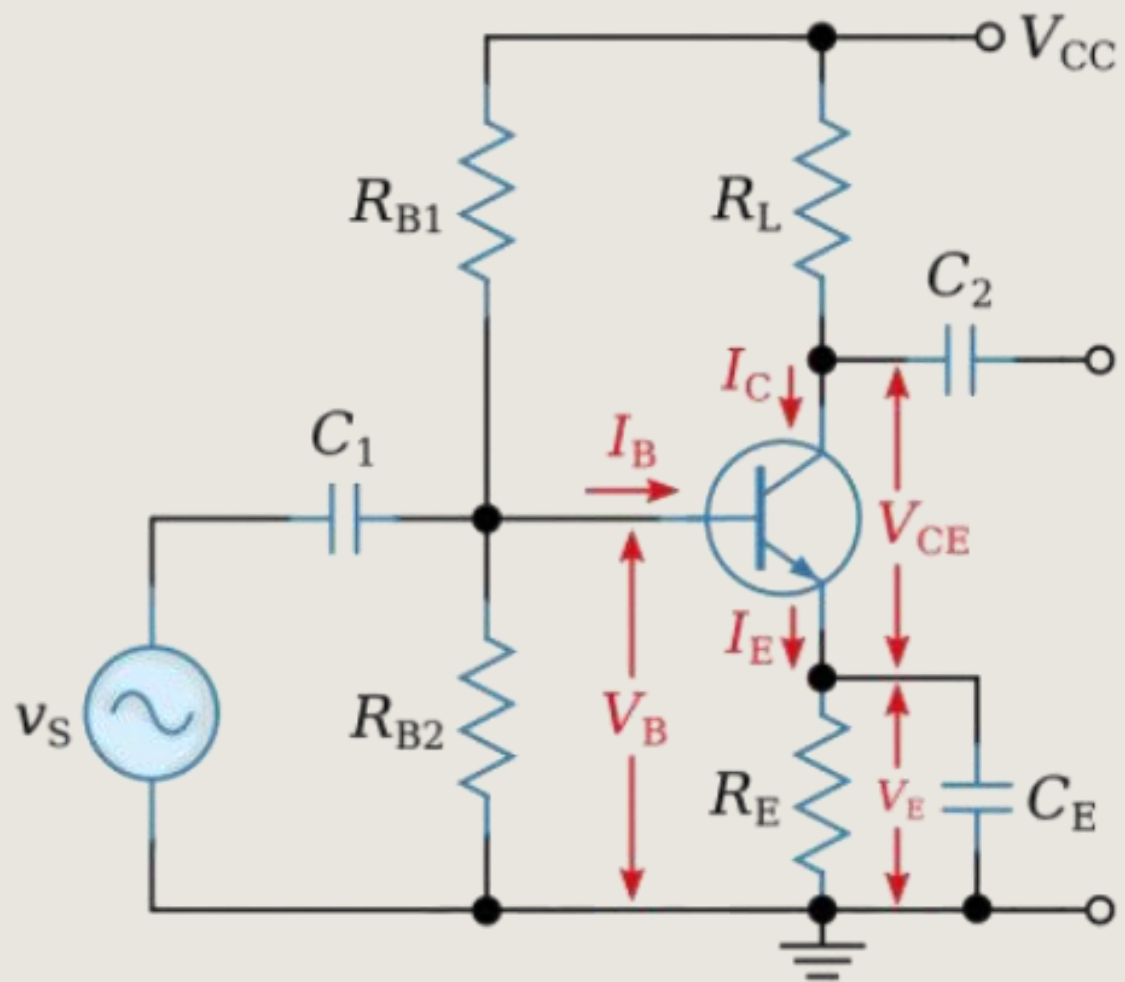

GAIN STAGE



WORKING PRINCIPLE


- The gain stage consists of a single stage CE Amplifier(common emitter).
- This configuration is chosen as it can handle inputs in the range of hundreds of millivolts.
- It helps in matching high input impedance and moderate output impedance.
- Gain Amplification improves the quality of Audio at speaker.


CALCULATIONS

GAIN STAGE : CE Amplifier

$$\text{Gain} = \frac{g_m R_c}{1 + g_m R_e} \approx \frac{R_c}{R_e} \quad (\text{assuming } g_m R_e \gg 1)$$
$$55 \approx \frac{18k}{330} = \frac{R_c}{R_e}$$
$$\text{Total cumulative gain} = 55 \cdot (11) \approx 550 \geq 500$$
$$V_{in} = V_B$$
$$I_c = I_s e^{\frac{V_B - V_E}{V_T}} \quad I_c \propto V_{in}$$
$$V_{out} = V_{DD} - I_c R_c$$
$$= \propto \frac{1}{I_c}$$
$$V_{out} \propto \frac{1}{V_{in}} \quad (\text{phase shift of } 180^\circ)$$

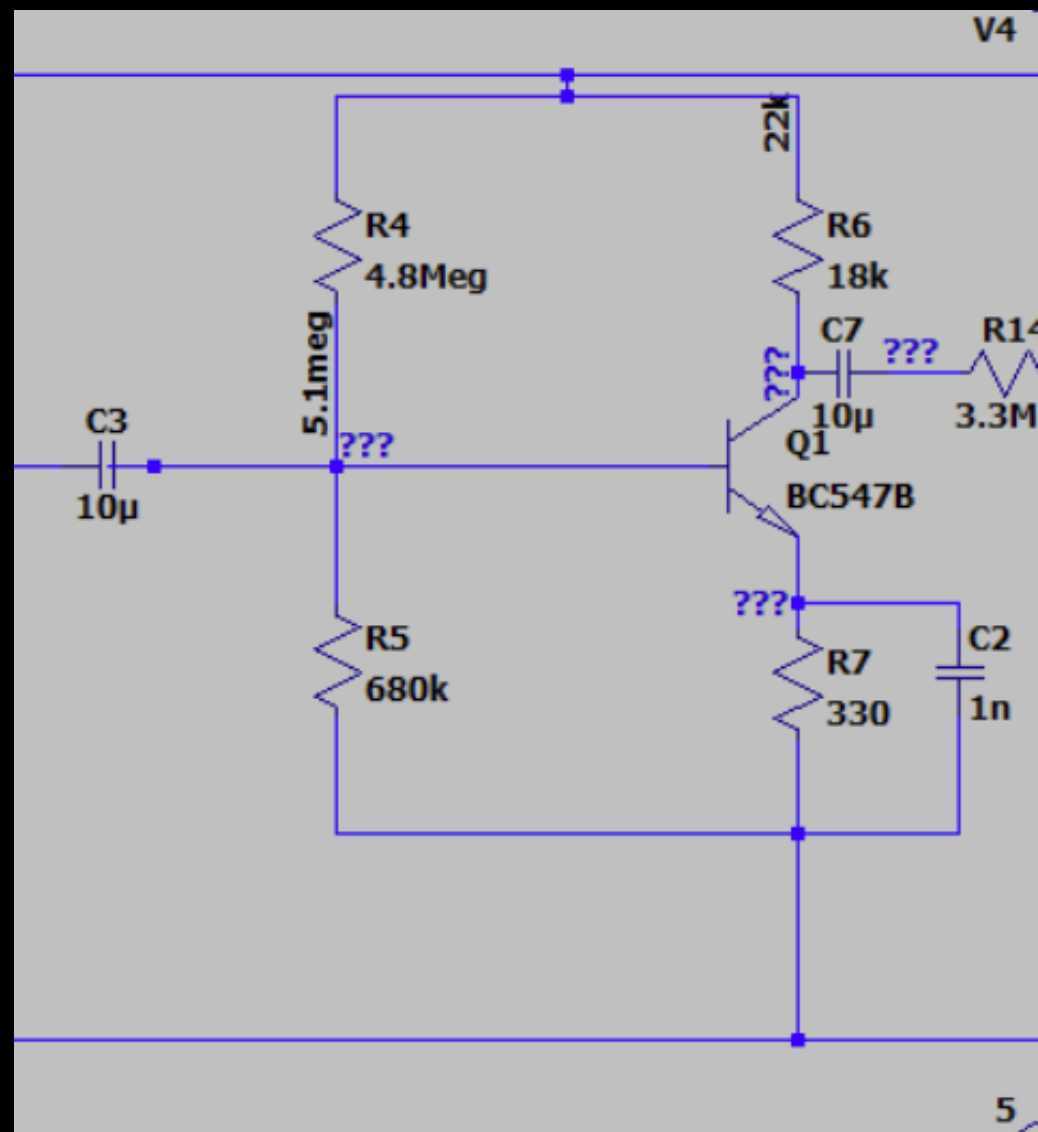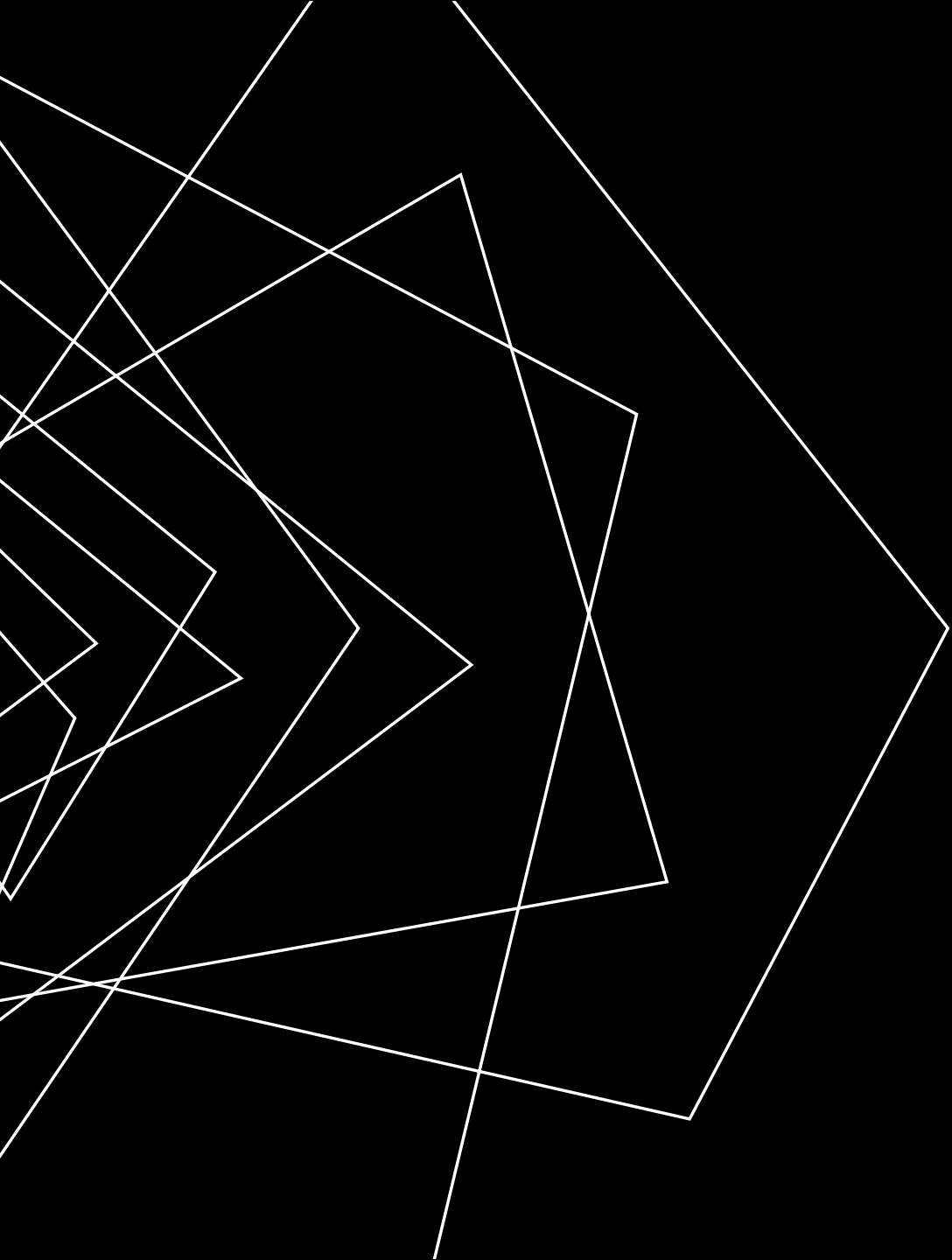

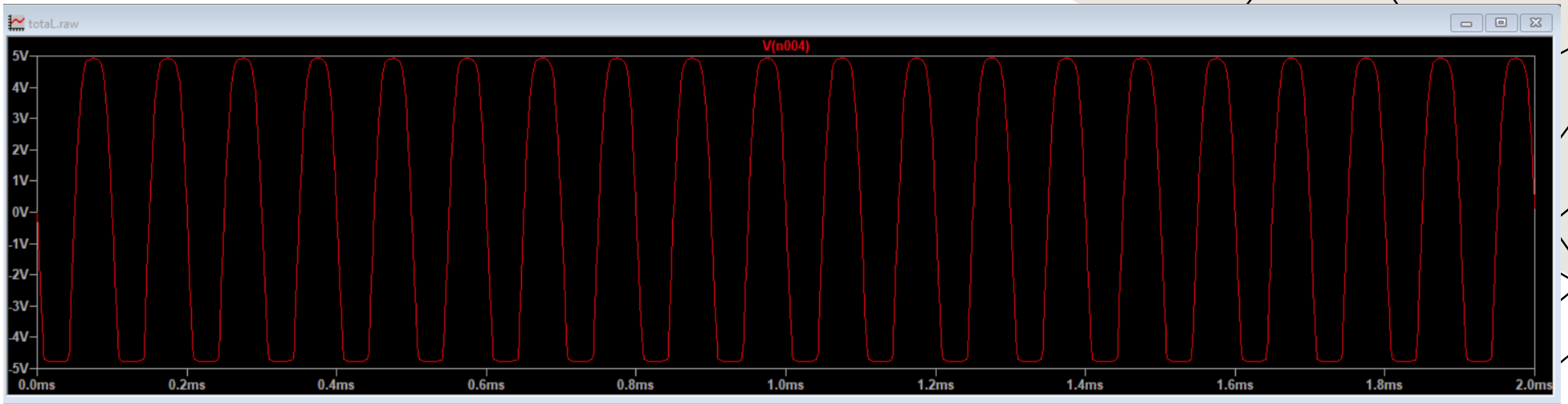

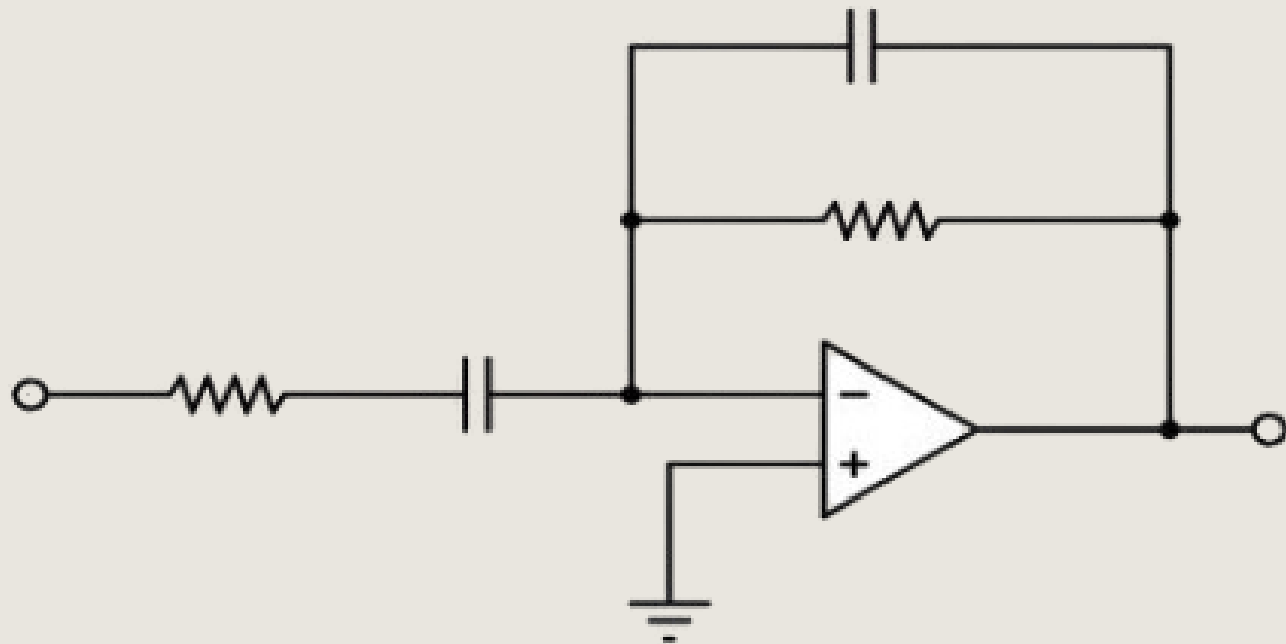

**ACTIVE
BANDPASS
FILTER**

WORKING PRINCIPLE

- Here we have designed an active bandpass filter which is inverting in nature.
- We have designed a bandpass filter because the audio should only be audible if it lies in the human hearing range.
- Filter stage removes the unnecessary interference of noise signals and also improves the overall efficiency of the audio signal which leads to better sound quality.
- The Band pass filter consists of a low pass filter and a high pass filter.
- Active filter can be cascaded without loading and impedance matching issues.
- Although the signals out of range are not audible they still interfere with the signal quality therefore removing them becomes essential.
- The HPF should pass signals whose frequency is above 2kHz and LPF should pass signals whose frequency is below 20kHz.

CALCULATIONS

$$f_L = \frac{1}{2 \cdot \pi \cdot R \cdot C_1}$$



$$\frac{1}{2 \cdot \pi \cdot 3.3 \cdot 10^6 \cdot 3 \cdot 10^{-9}}$$



$$= 16.07625688$$




$$f_H = \frac{1}{2 \cdot \pi \cdot R \cdot C_2}$$




$$\frac{1}{2 \cdot \pi \cdot 3.3 \cdot 10^6 \cdot 2.2 \cdot 10^{-12}}$$


$$= 21922.16847$$

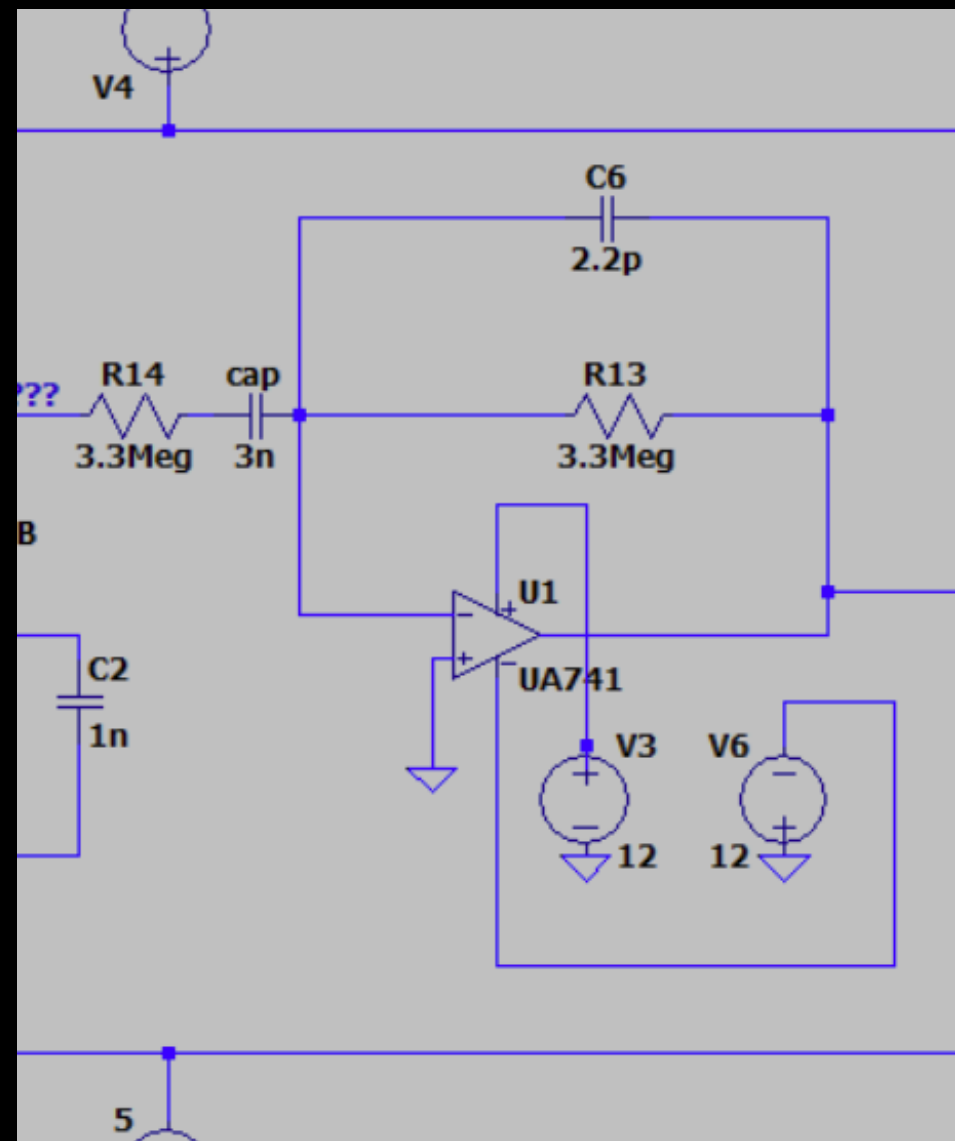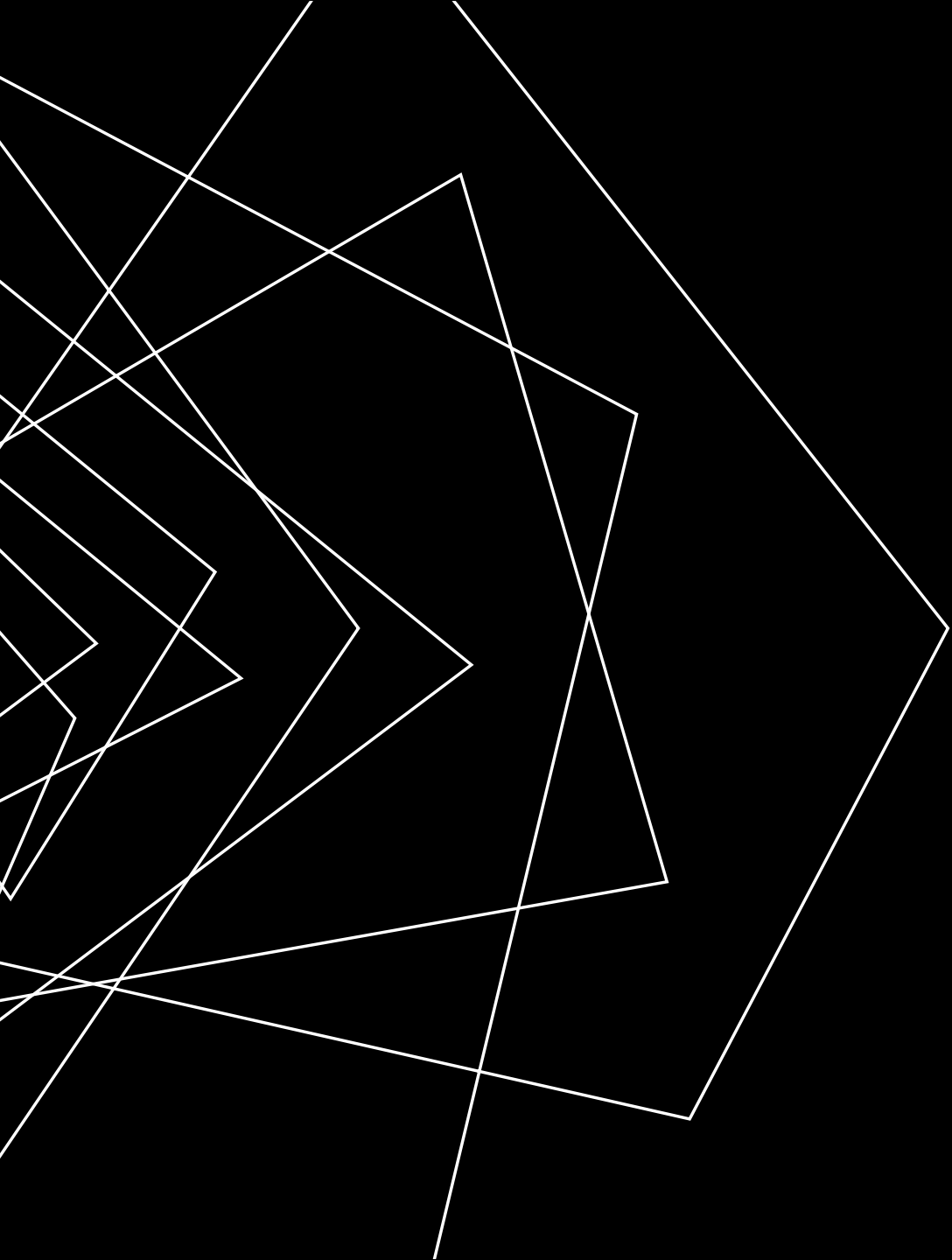

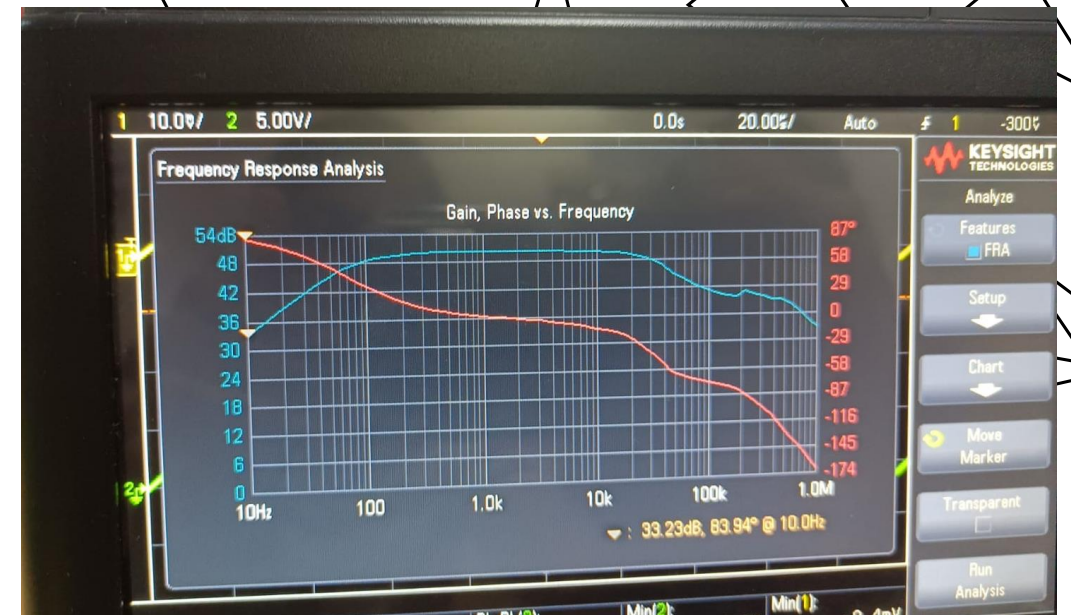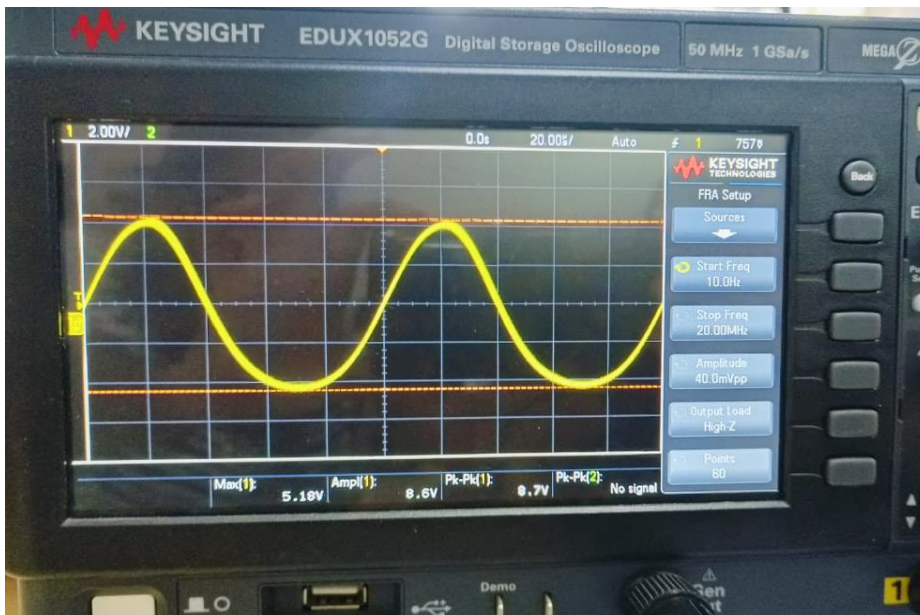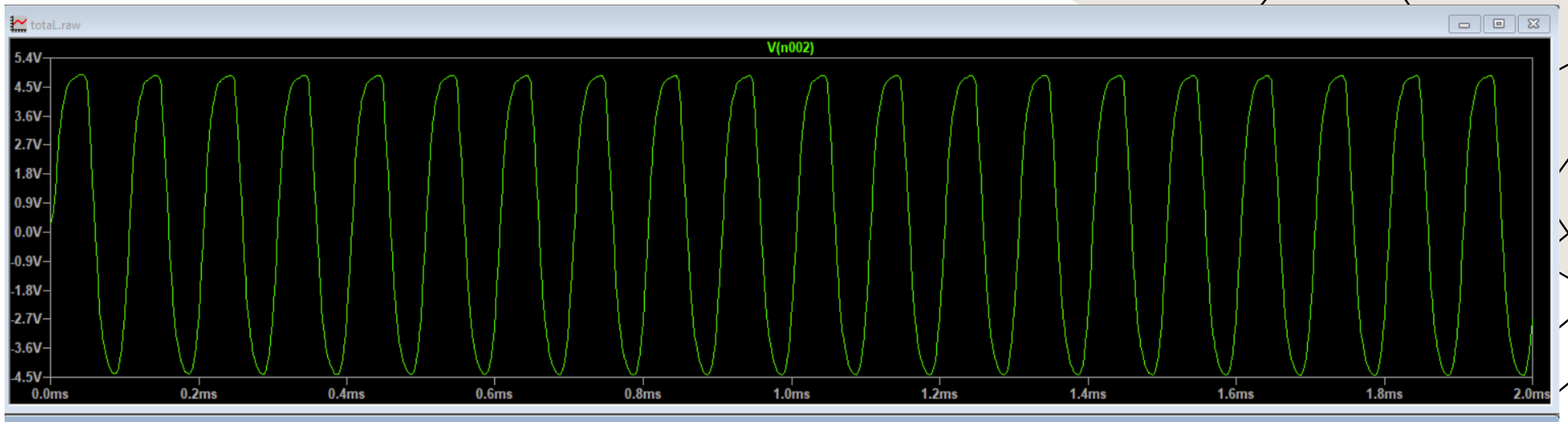

AC ANALYSIS

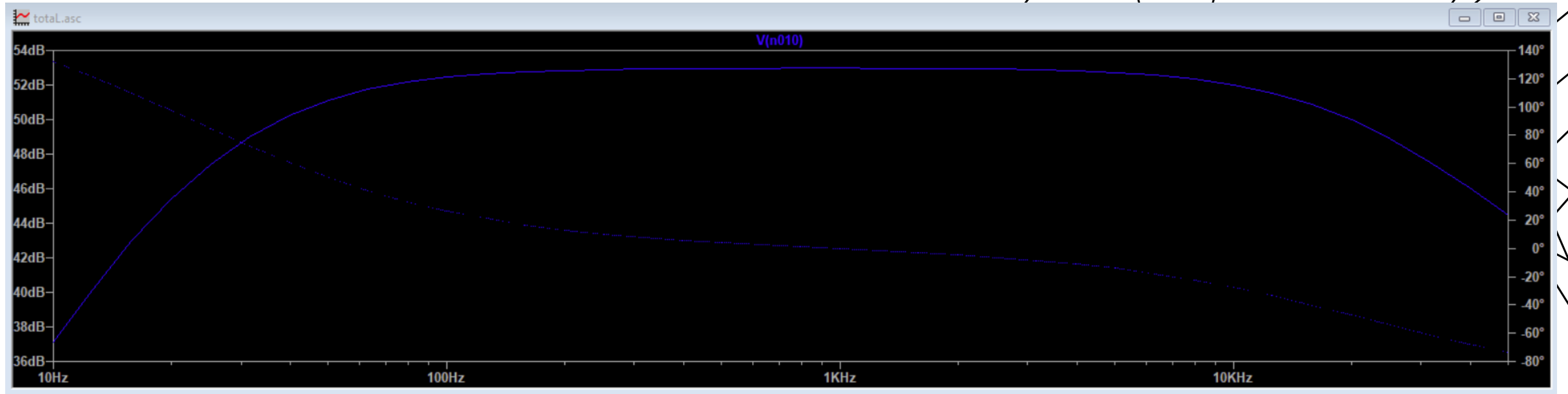

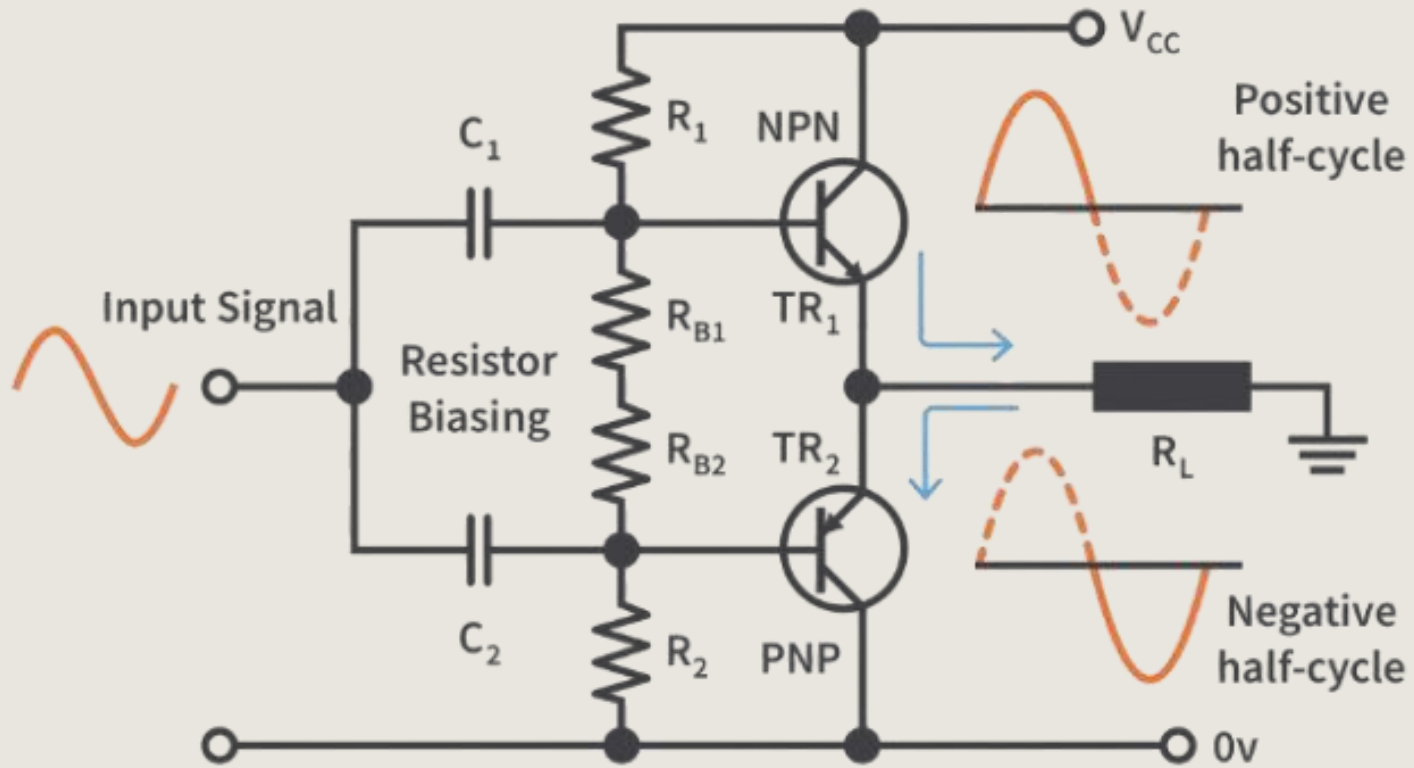

**POWER
AMPLIFIER**

TYPES OF POWER AMPLIFIERS

- **Class A amplifier:** The biasing conditions in class A power amplifier are such that the collector current flows for the entire AC signal applied.
- **Class B amplifier:** The biasing conditions in class B power amplifier are such that the collector current flows for the half cycle of input AC signal applied.
- **Class AB amplifier:** The class AB power amplifier is one which is created by combining both class A and class B in order to have all the disadvantages of both the classes and to minimize the problems they have.

WORKING PRINCIPLE

- Here for the power amplifier stage , we have used class AB emitter – follower configuration.
- It provides sufficient power to an output load to drive other power device.
- It is chosen as it gives low cross-over distortion.
- In previous stages, the voltage has been amplified .The current is yet to be amplified as the signal at the output needs certain threshold amount of power to be able to drive the speaker.
- It provides a low output resistance in order to avoid loss of gain and to maintain linearity (to minimize harmonic distortion).

CALCULATIONS

POWER AMP

$$I_d = \frac{V_{CC} - 1.4}{R_1 + R_2} = \frac{3.6}{R_1 + R_2}$$



$$I_d \approx 1 \text{ mA}$$



(assume)

$$2R_1 = \frac{3.6}{1 \text{ mA}}$$


$$R_1 = R_2 = 1.8 \text{ k} \approx 2 \text{ k}$$

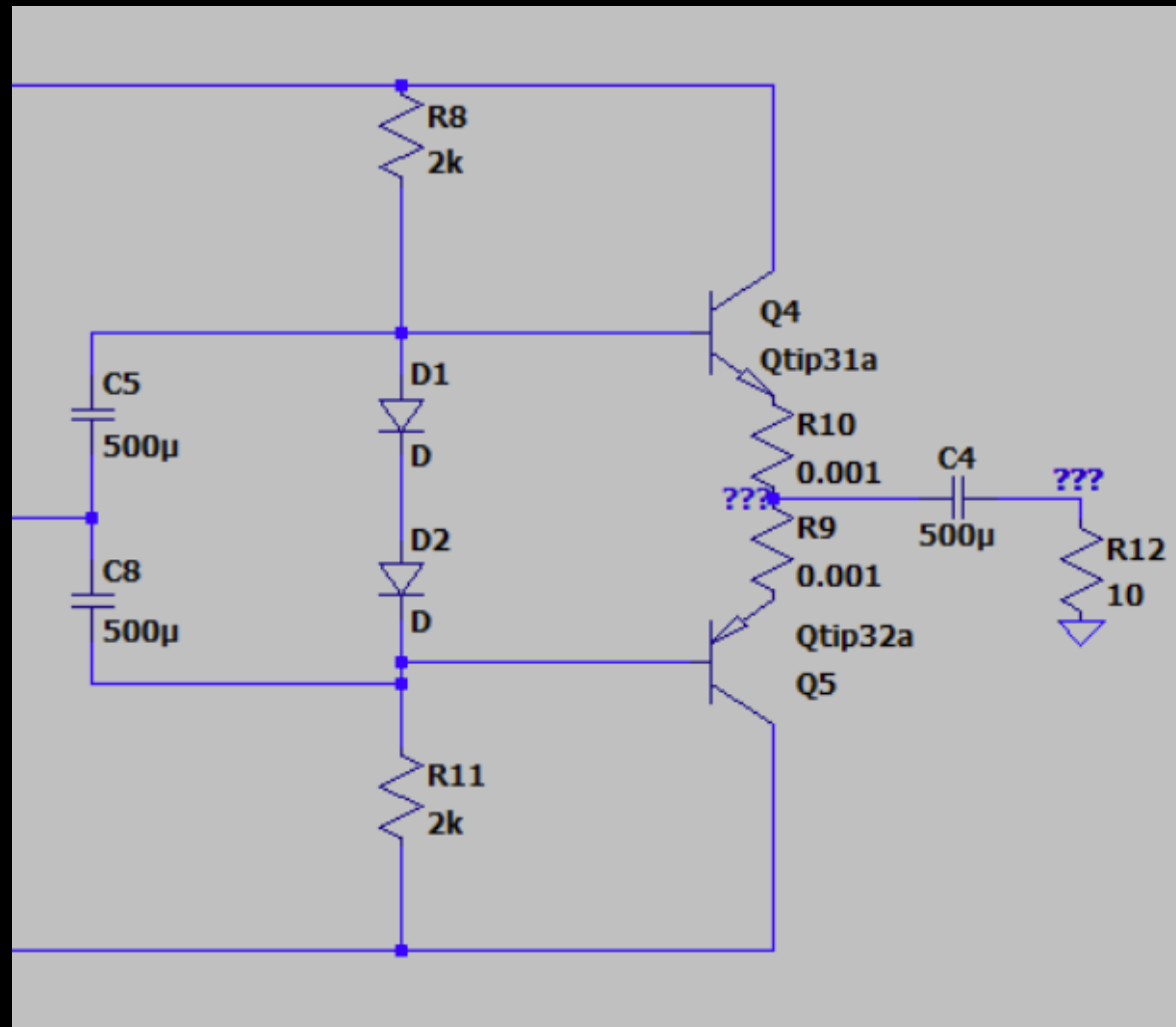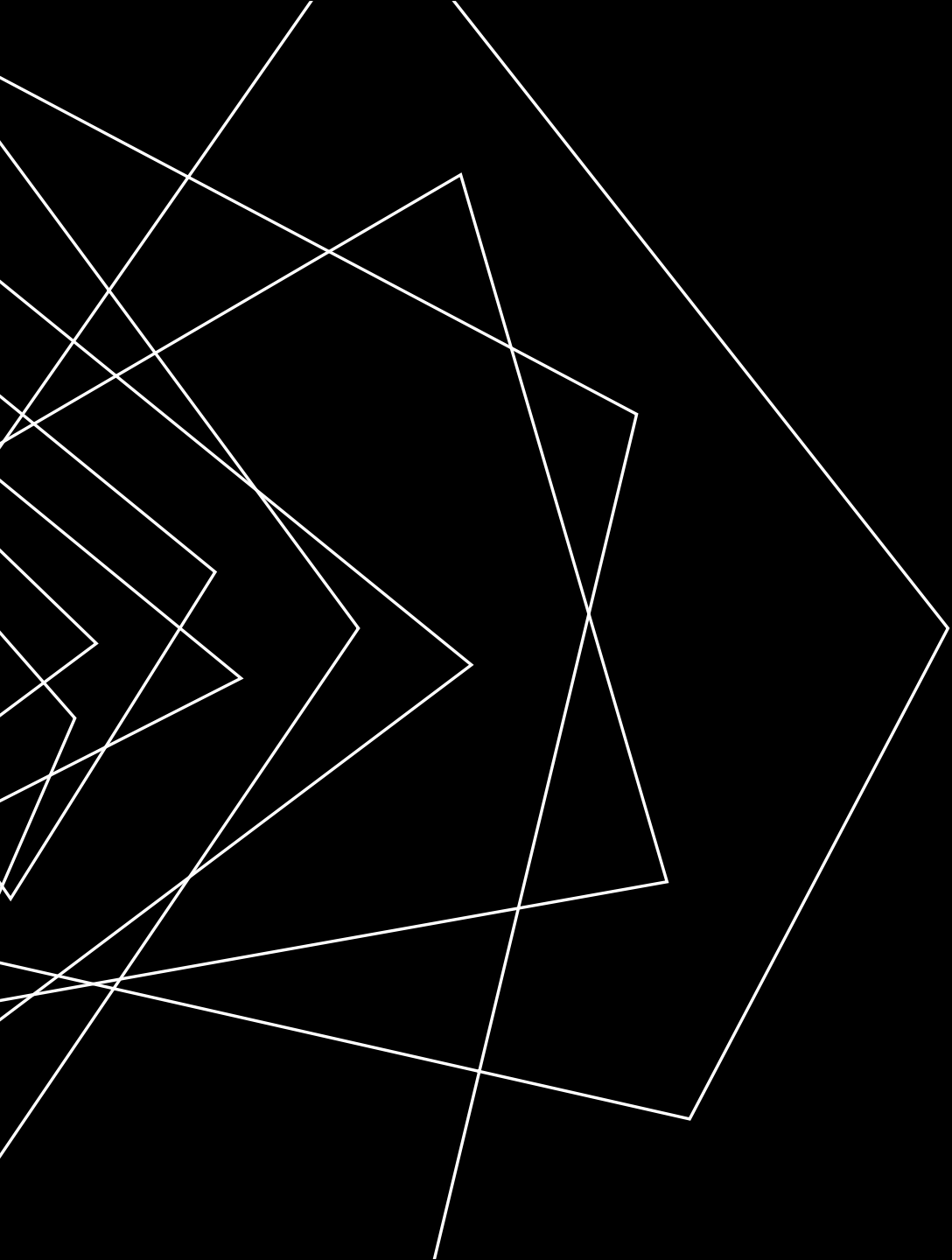$I_d \approx 1 \text{ mA}$ For ≈ 0.7 drop across diode
to turn both transistors ON



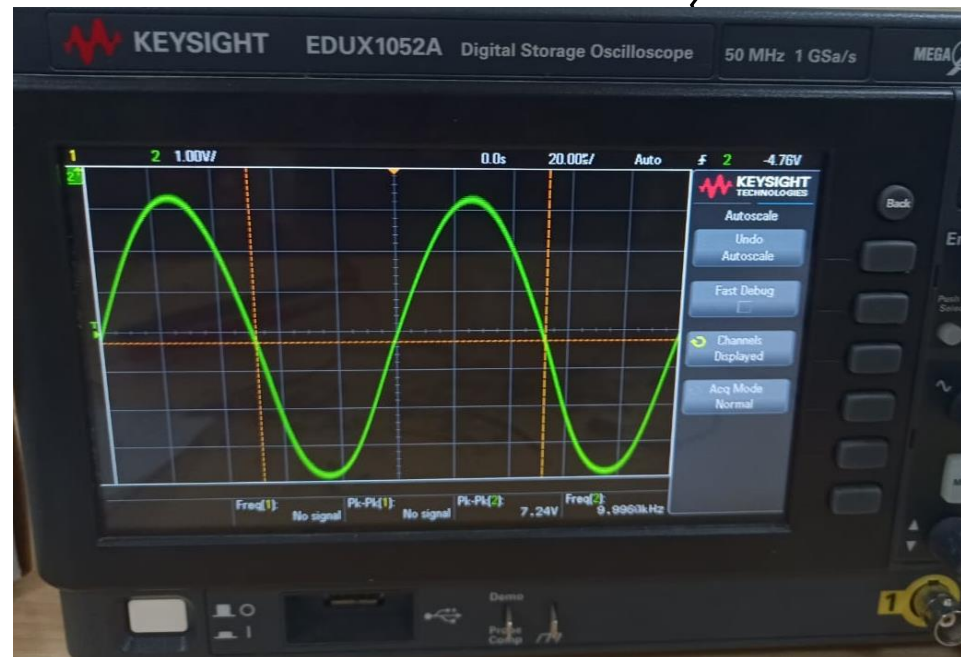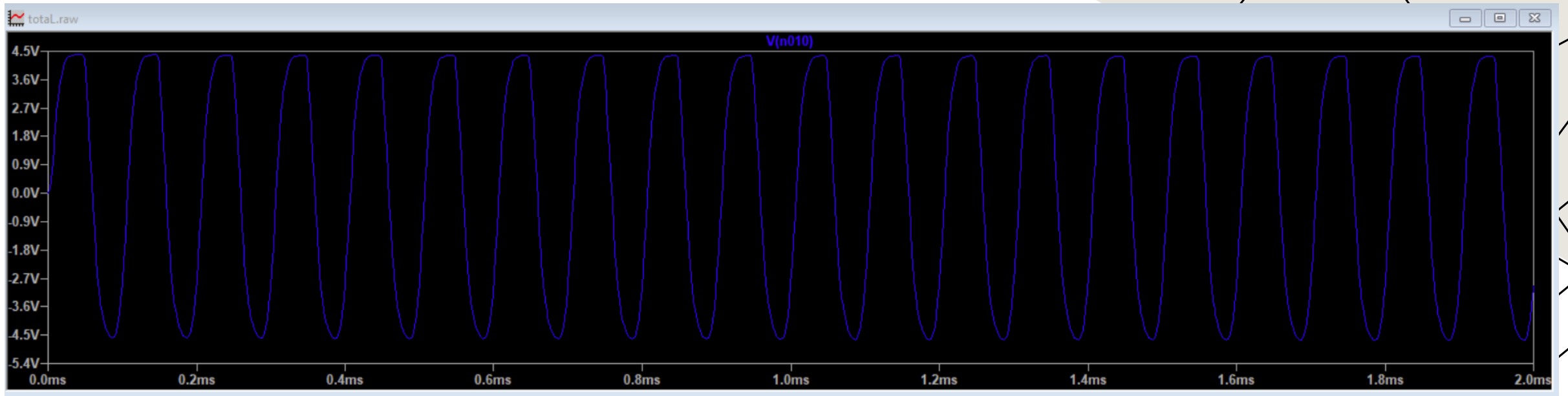

FINAL CIRCUIT

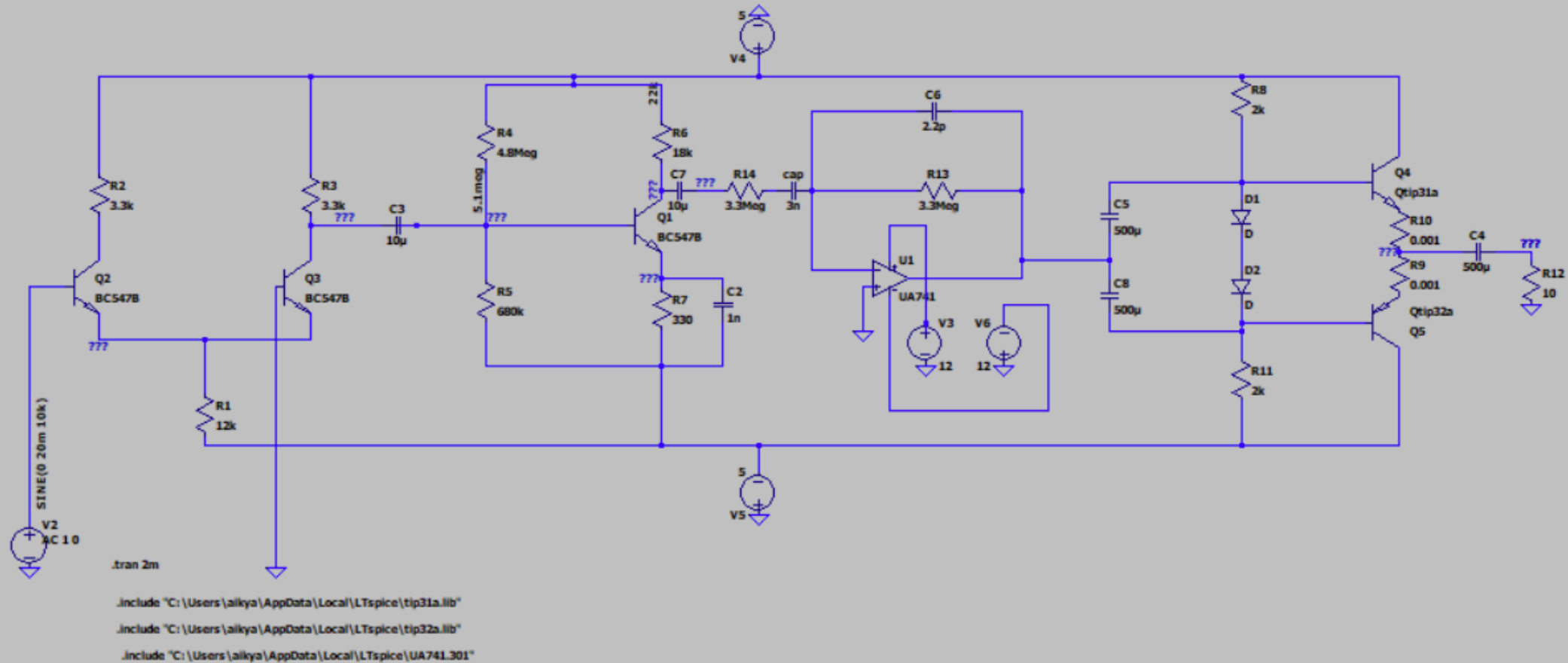

FINAL OUTPUT

